

EE236 : Electronic Devices Lab

Lab 0 [Tuesday Batch]

Prajwal Nayak (22B4246)

August 4, 2024

1 Objectives

- Installing NGSPICE and getting familiar with using it.
- Learning the basic commands to design circuits, transient analysis, including external files and using them as a component in a larger circuit and plotting graphs
- Using NanoHub for analysis of characteristics of PN junctions.

2 Circuit analysis using NGSPICE

2.1 Transient analysis of RC Circuit

2.1.1 Circuit


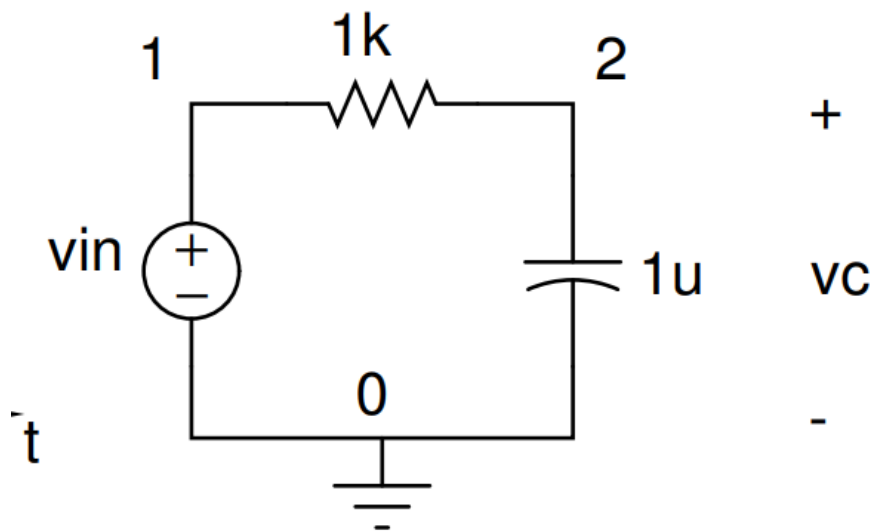


Figure 1: RC Circuit

2.1.2 Code

```
1 RC Circuit Transient Response
2 *resistor connected between nodes 1 and 2
3 r1 1 2 1k
4 *capacitor connected between nodes 2 and 0
5 c1 2 0 1u
6 *piecewise linear input voltage
7 vin 1 0 pw1 (0 0 10ms 0 11ms 5v 20ms 5v)
8 *transient analysis for 20ms, step size 0.02ms
9 .tran 0.02ms 20ms
10 *defining the run-time control functions
11 .control
12 run
13 *plotting input and output voltages
14 plot v(1) v(2)
15 .endc
16 .end
```

2.1.3 Plots


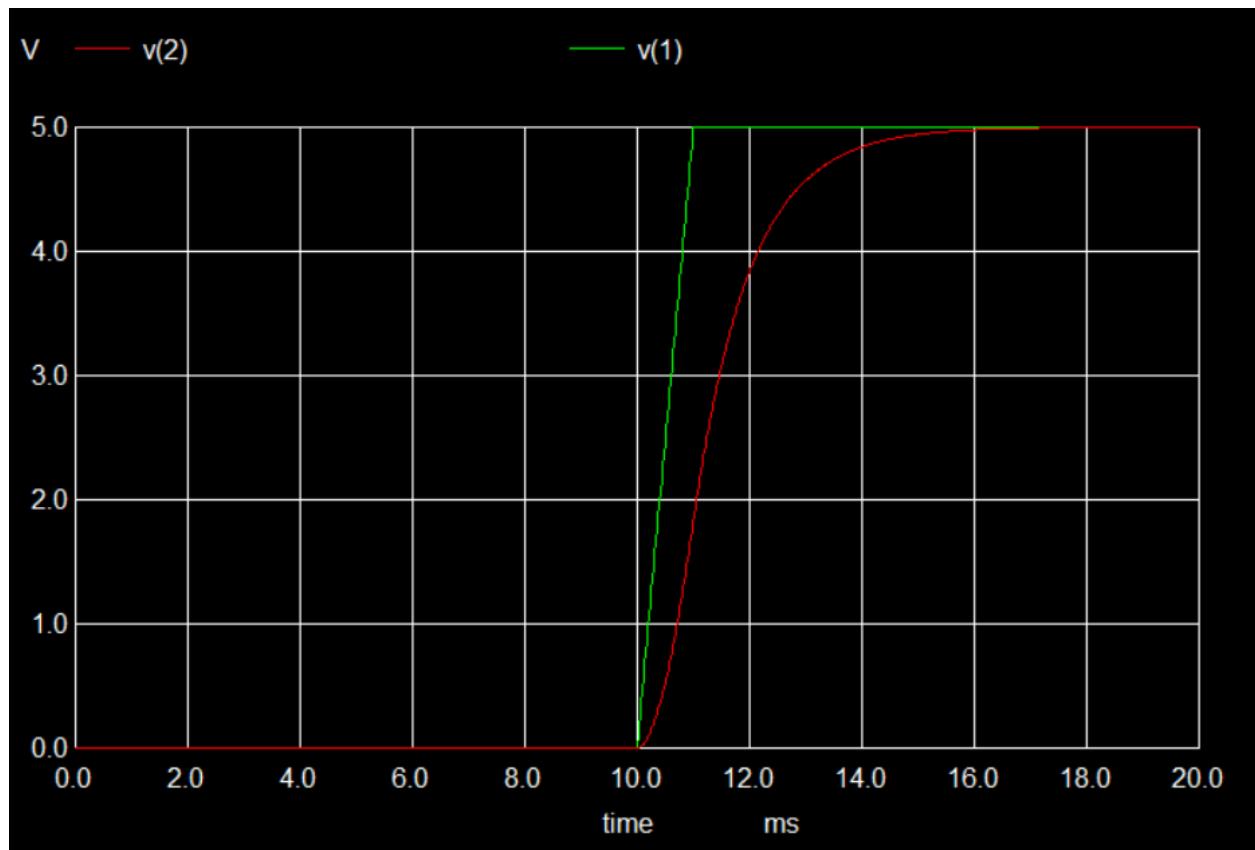


2.2 AC analysis of RC Circuit

2.2.1 Code

```
1 RC Circuit Frequency Response
2 r1 1 2 1k
3 c1 2 0 1u
4 *Specifying an AC source with zero dc
5 vin 1 0 dc 0 ac 1
6 *AC analysis for 1 Hz to 1MHz, 10 points per decade
7 .ac dec 10 1 1Meg
8 .control
9 run
10 *Magnitude dB plot for v(2) on log scale
11 plot vdb(2) xlog
12 *Phase degrees plot for v(2) on log scale
13 plot {57.29*vp(2)} xlog
14 .endc
15 .end
```

2.2.2 Plots

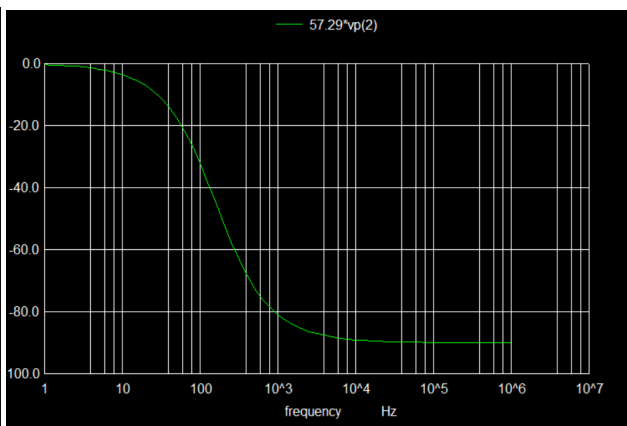
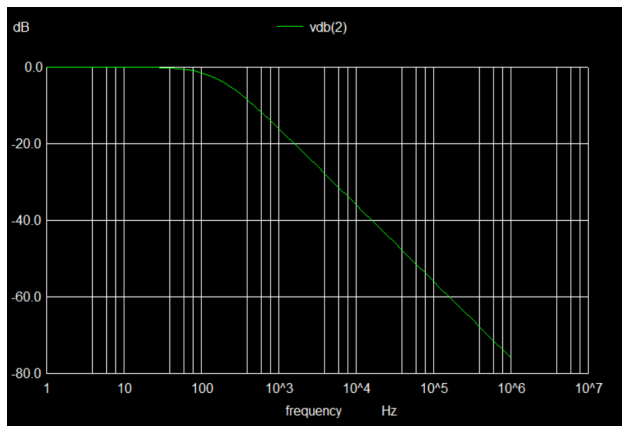


2.3 DC Analysis of Shunt Clipper

2.3.1 Code

```
1 Shunt Clipper DC analysis
2 r1 1 2 1k
3 *Specifying a default diode p n
4 d1 2 3 di
5 .model di D()
6 *Independent DC source of 2V
7 vdc 3 0 dc 2
8 *Independent DC source whose voltage is to be varied
9 vin 1 0 dc 0
10 *DC Analysis on source vin, to vary from -5 to +5V
11 .dc vin -5 5 0.01
12 .control
13 run
14 plot v(2) vs v(1)
15 .endc
```

2.3.2 Circuit and Plot

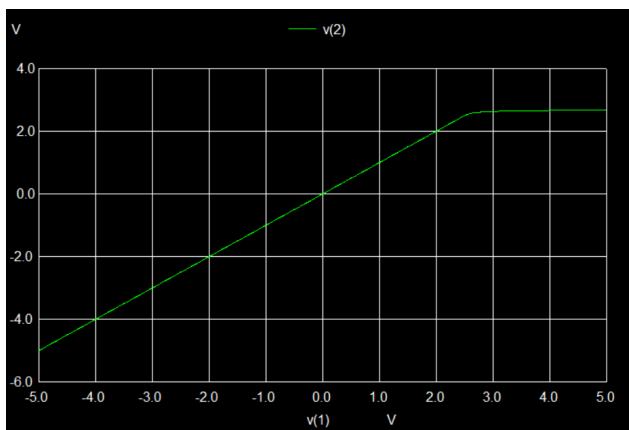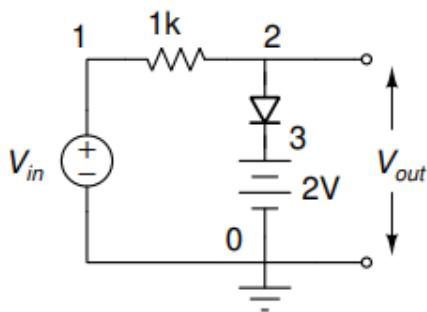

2.4 Using Subcircuits

2.4.1 Code

```
1 *Defining the Subcircuit RC subcircuit: <name> <pin1> <pin2> <pin3>
2 .subckt RC_subcircuit IN OUT COM
3 r IN OUT 1K
4 c OUT com 1u
5 .ends
```

```

6 *Subcircuit definition ends here
7 vsin INPUT gnd sin(0 2.5 1K 0 0)
8 *Invoking RC_subcircuit with an
9 xrc1 INPUT 1 gnd RC_subcircuit
10 xrc2 1 2 gnd RC_subcircuit
11 xrc3 2 OUTPUT gnd RC_subcircuit
12 .control
13 tran 0.02m 40m
14 plot v(INPUT) v(OUTPUT)
15 .endc
16 .end


```

```


1 RC Circuit Transient Analysis using Subcircuits
2 *Providing some default component values
3 .subckt RC_subcircuit IN OUT COM r1 = 1k c1 = 1u
4 r IN OUT {r1}
5 c OUT COM {c1}
6 .ends
7 vsin INPUT gnd sin(0 2.5 1k 0 0)
8 xrc1 INPUT 1 gnd RC_subcircuit
9 *Instantiating component values for 2nd subcircuit
10 xrc2 1 2 gnd RC_subcircuit r1 = 100 c1 = 0.1u
11 xrc3 2 OUTPUT gnd RC_subcircuit
12 .control
13 tran 0.02m 40m
14 plot v(INPUT) v(OUTPUT)
15 .endc
16 .end

```


2.4.2 Circuit

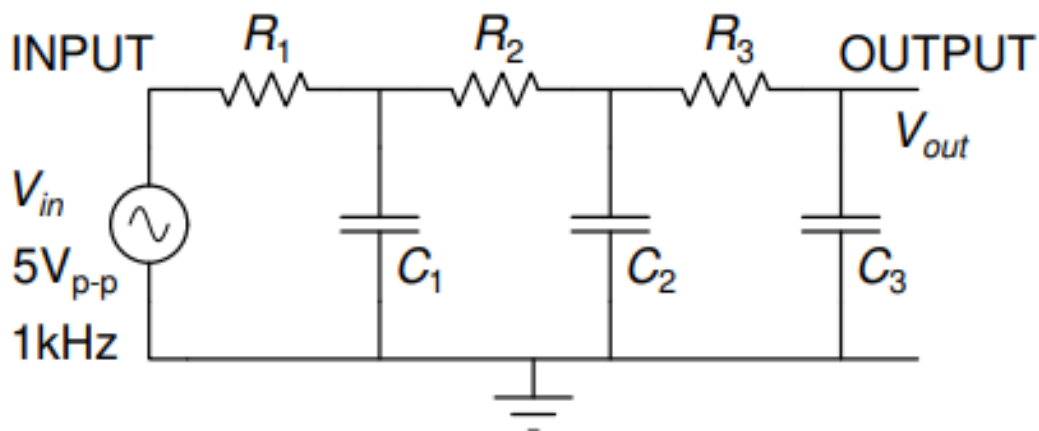

2.4.3 RC subcircuit

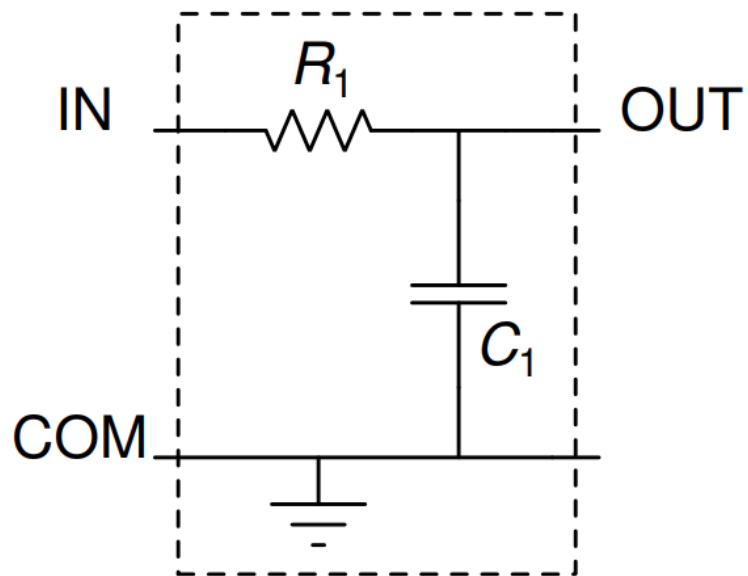


2.4.4 Plot

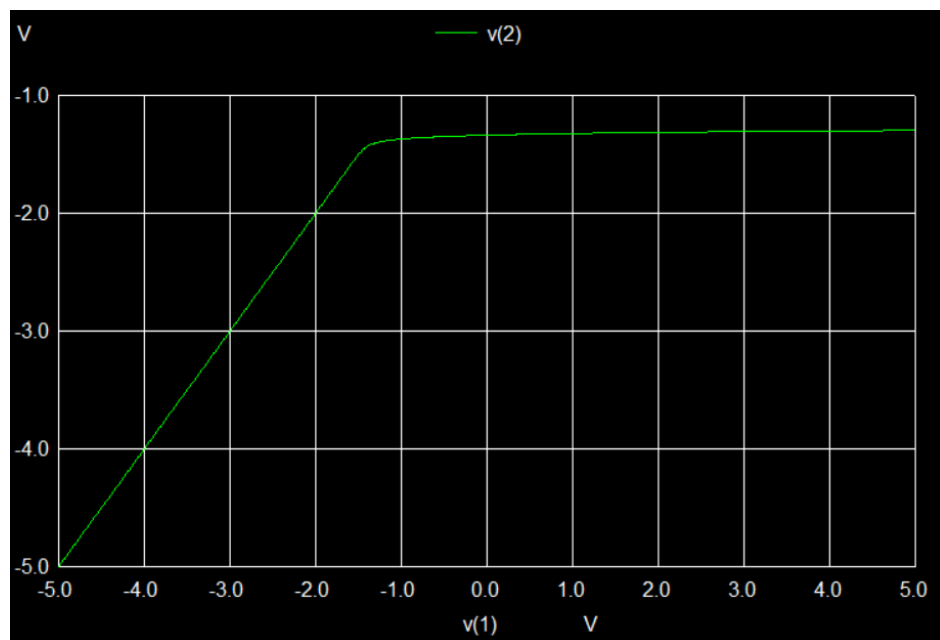


2.5 Using component defined in an external file

2.5.1 Circuit

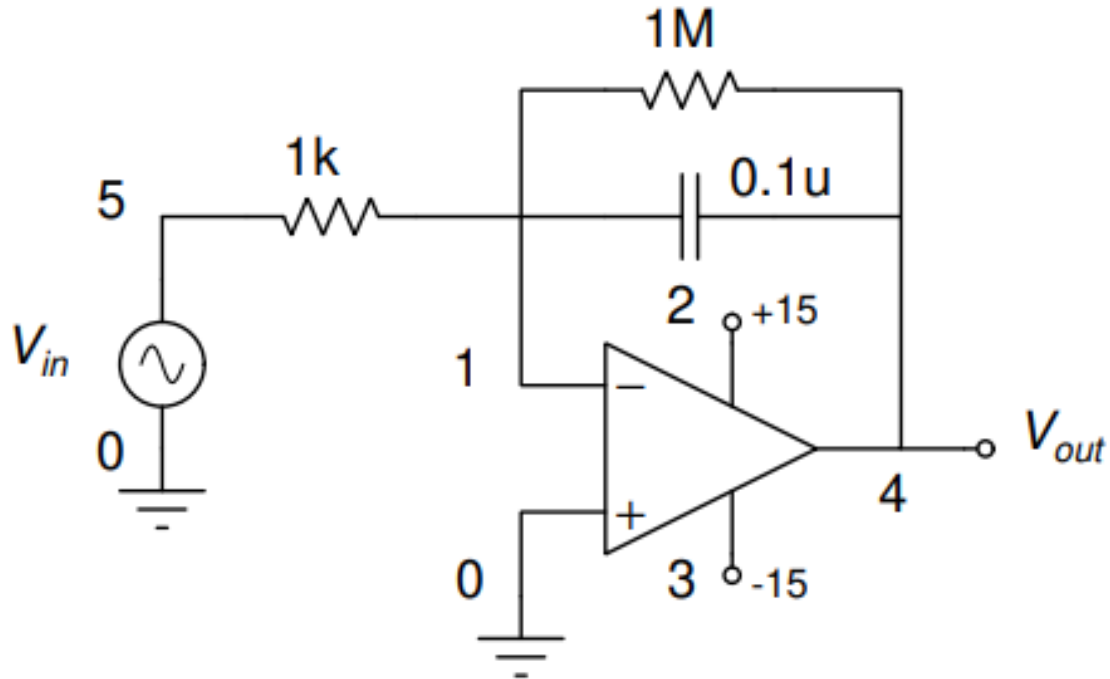

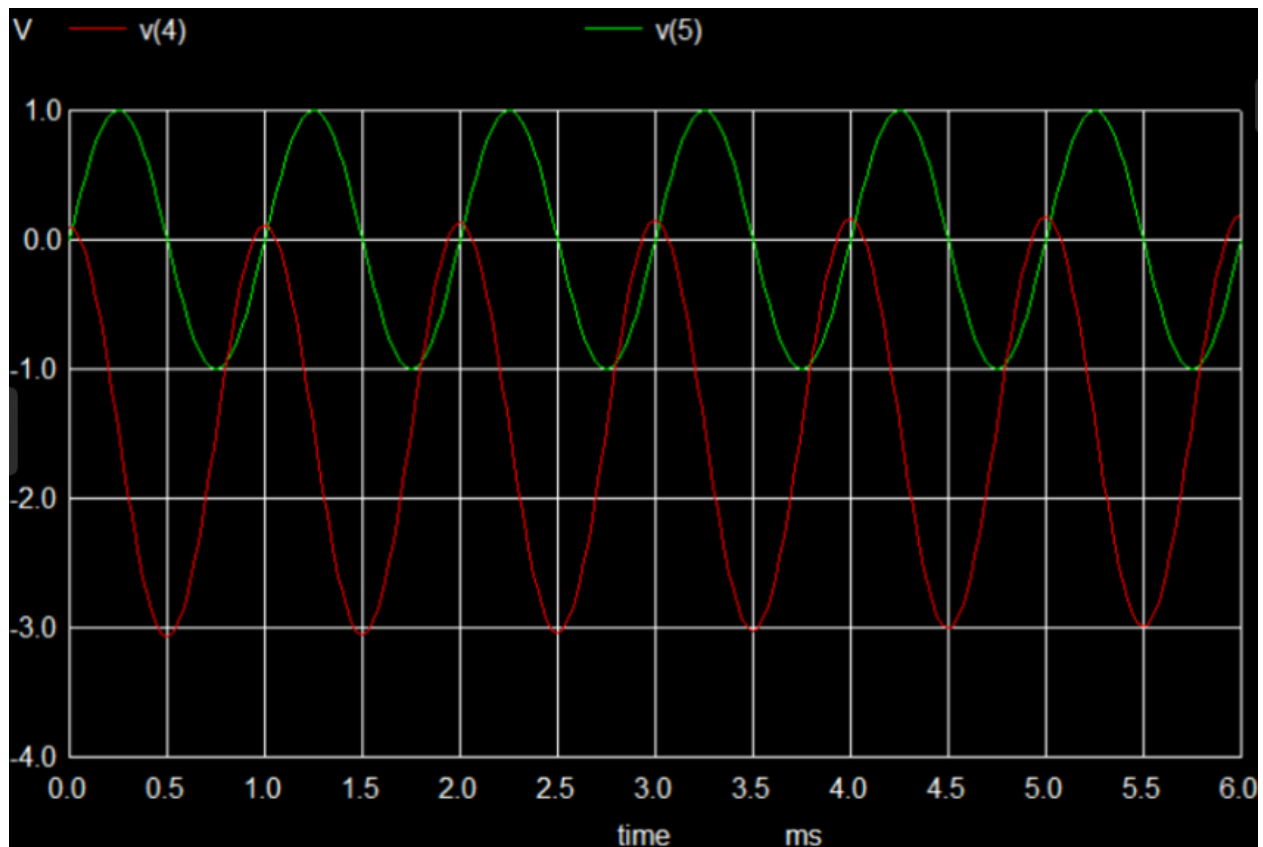2.5.2 Code

```
1 RC Circuit Transient Analysis using Subcircuits
2 *Providing some default component values
3 .subckt RC_subcircuit IN OUT COM r1 = 1k c1 = 1u
4 r IN OUT {r1}
5 c OUT COM {c1}
6 .ends
7 vsin INPUT gnd sin(0 2.5 1k 0 0)
8 xrc1 INPUT 1 gnd RC_subcircuit
9 *Instantiating component values for 2nd subcircuit
10 xrc2 1 2 gnd RC_subcircuit r1 = 100 c1 = 0.1u
11 xrc3 2 OUTPUT gnd RC_subcircuit
12 .control
13 tran 0.02m 40m
14 plot v(INPUT) v(OUTPUT)
15 .endc
16 .end
```



2.5.3 Plot

2.6 Exercises

1. Consider the shunt clipper shown in Example III. Change the following and simulate to observe V_{out} v/s V_{in} variation. For each case, give a 1 kHz sinusoidal input and observe the output waveform (six cycles):

(a) The diode connections

Solution:

Code:

```

1 Shunt Clipper DC analysis
2 r1 1 2 1k
3 *Specifying a default diode p n
4 d1 3 2 di
5 .model di D()
6 *Independent DC source of 2V
7 vdc 3 0 dc 2
8 *Independent DC source whose voltage is to be varied
9 vin 1 0 sin (0 5v 1k 0 0)
10 .tran 0.01m 6m
11 .control

```




```

12 run
13 plot v(1) v(2)
14 .endc

```

Plot:

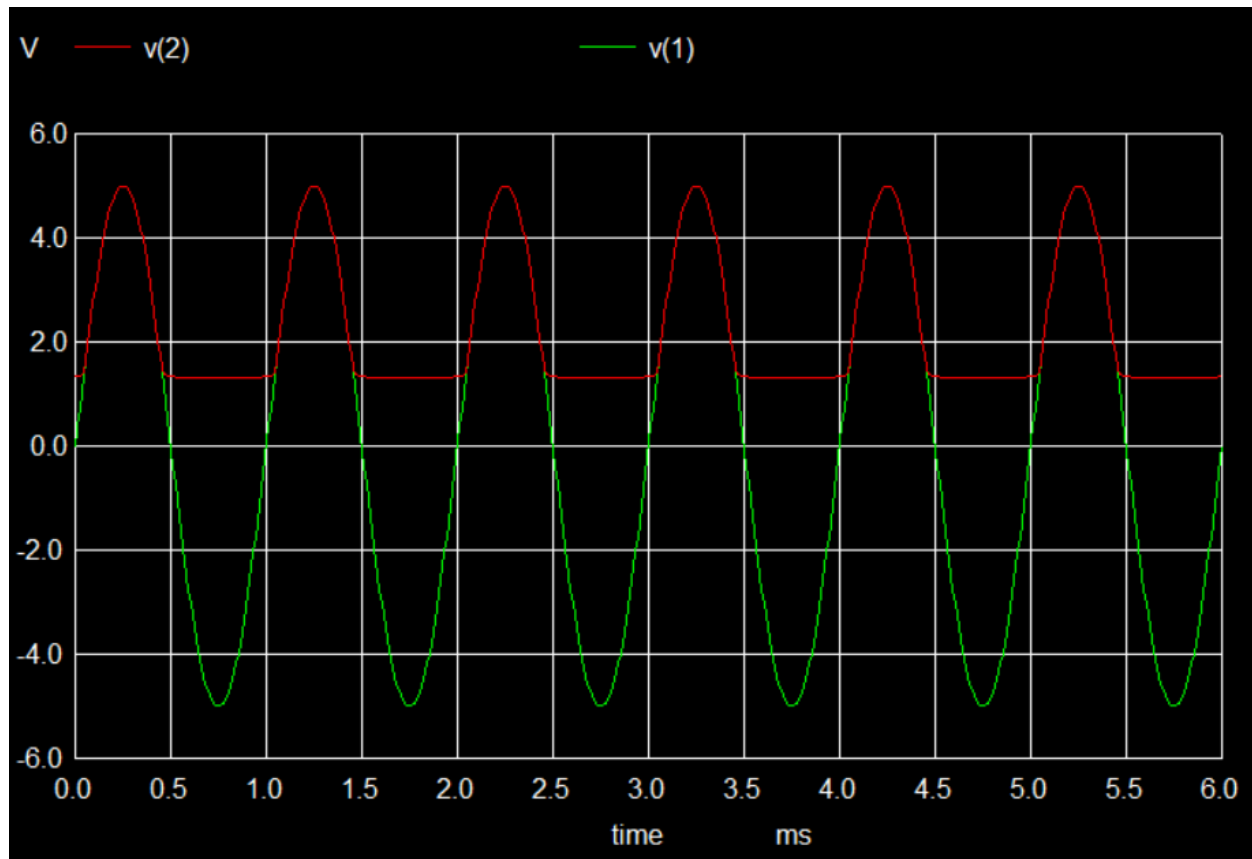

(b) The 2 V battery polarity Solution:

Code:


```

1 Shunt Clipper DC analysis
2 r1 1 2 1k
3 *Specifying a default diode p n
4 d1 2 3 di
5 .model di D()
6 *Independent DC source of 2V
7 vdc 0 3 dc 2
8 *Independent DC source whose voltage is to be varied
9 vin 1 0 sin (0 5v 1k 0 0)
10 .tran 0.01m 6m
11 .control
12 run
13 plot v(1) v(2)

```


```
14 .endc
```

Plot:

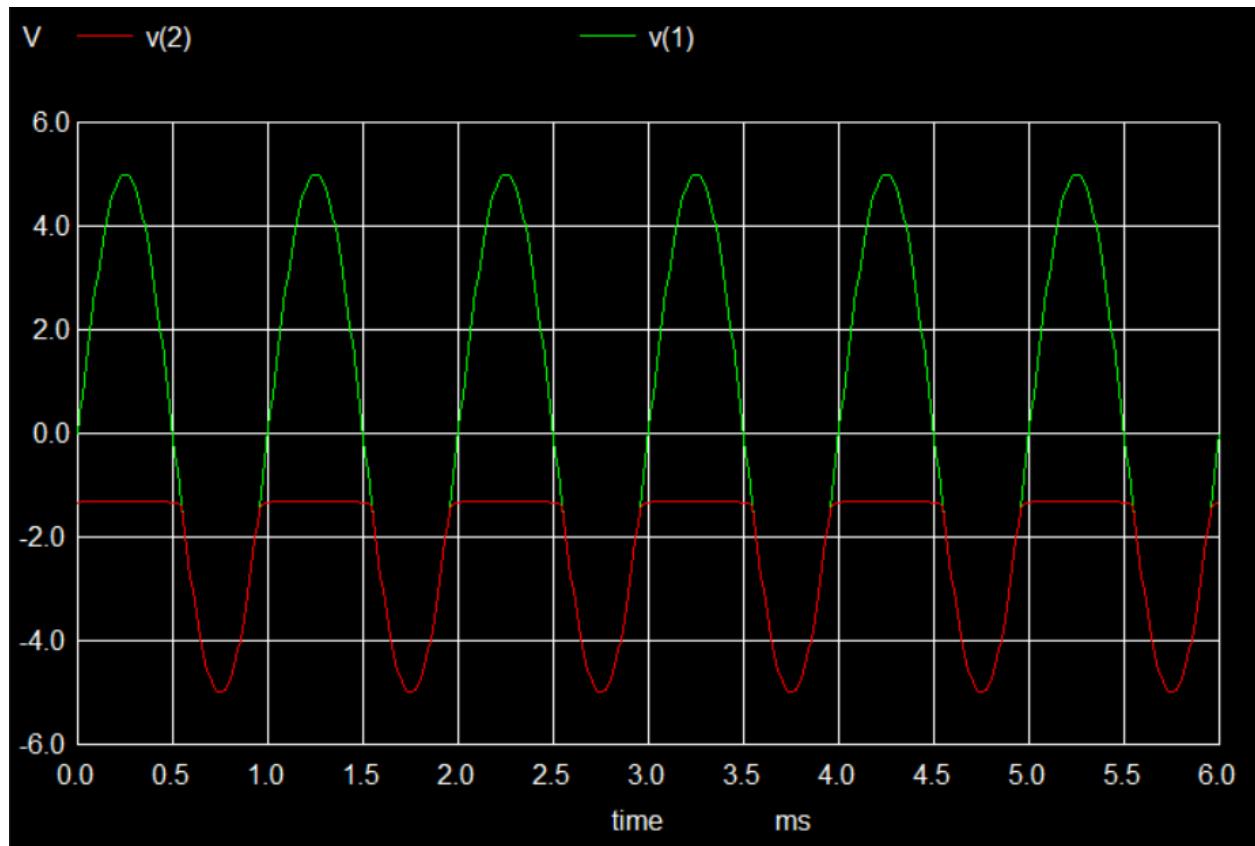

2. Write an NGSPICE netlist for a diode-based bridge rectifier and simulate it to observe the rectified voltage across a load resistor, by giving a 12 V, 50 Hz input. Also, observe the V_{out} v/s V_{in} transfer characteristics.

Circuit:

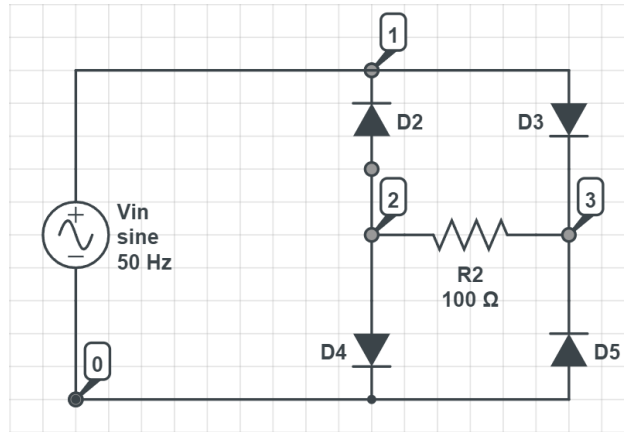


Code:

```

1 Bridge rectifier
2 d0 2 1 a
3 d1 2 0 a
4 d2 1 3 a
5 d3 0 3 a
6 .model a D()
7 r1 2 3 100
8 vin 1 0 sin (0 12v 50 0 0)
9 .tran 0.01m 100m
10 .control
11 run
12 plot v(3)-v(2) vs v(1)
13 .endc

```

Plot:

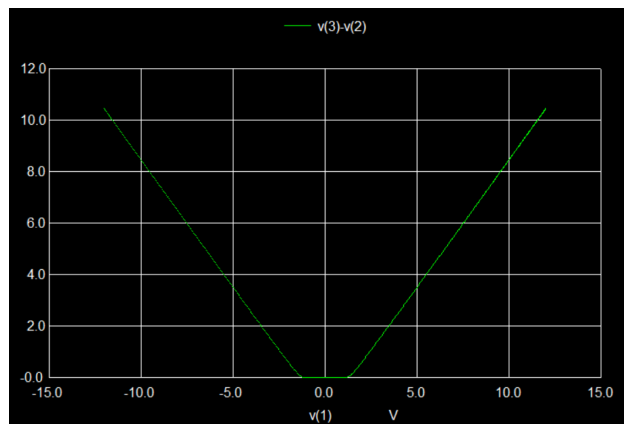

3 NanoHub

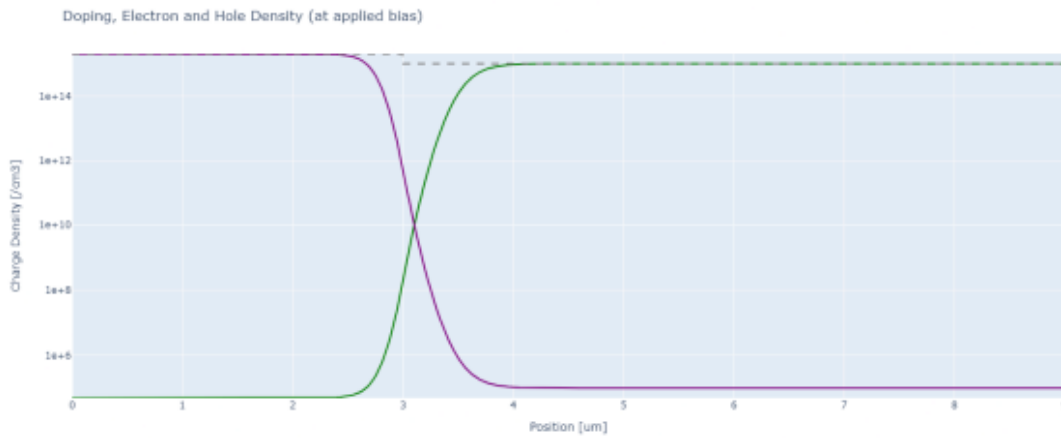


Figure 2: equilibrium

At non equilibrium, these are the plots:

1. Fermi level is different for holes and electrons
2. The electric field is reduced in magnitude due to reduction in depletion region
3. Number of minority carriers has increased on both p and n sides
4. There are 4 graphs each for equilibrium and non equilibrium

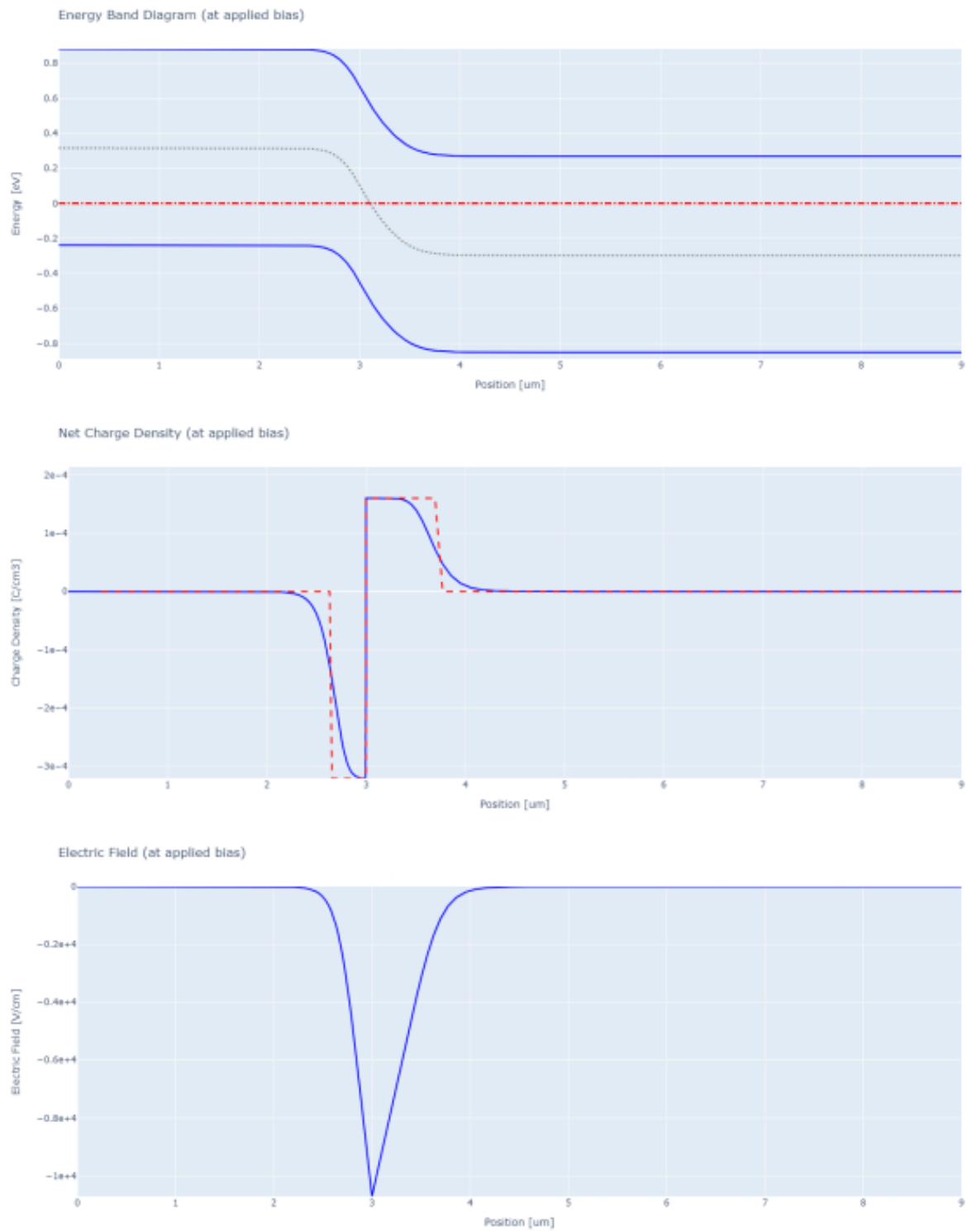


Figure 3: equilibrium

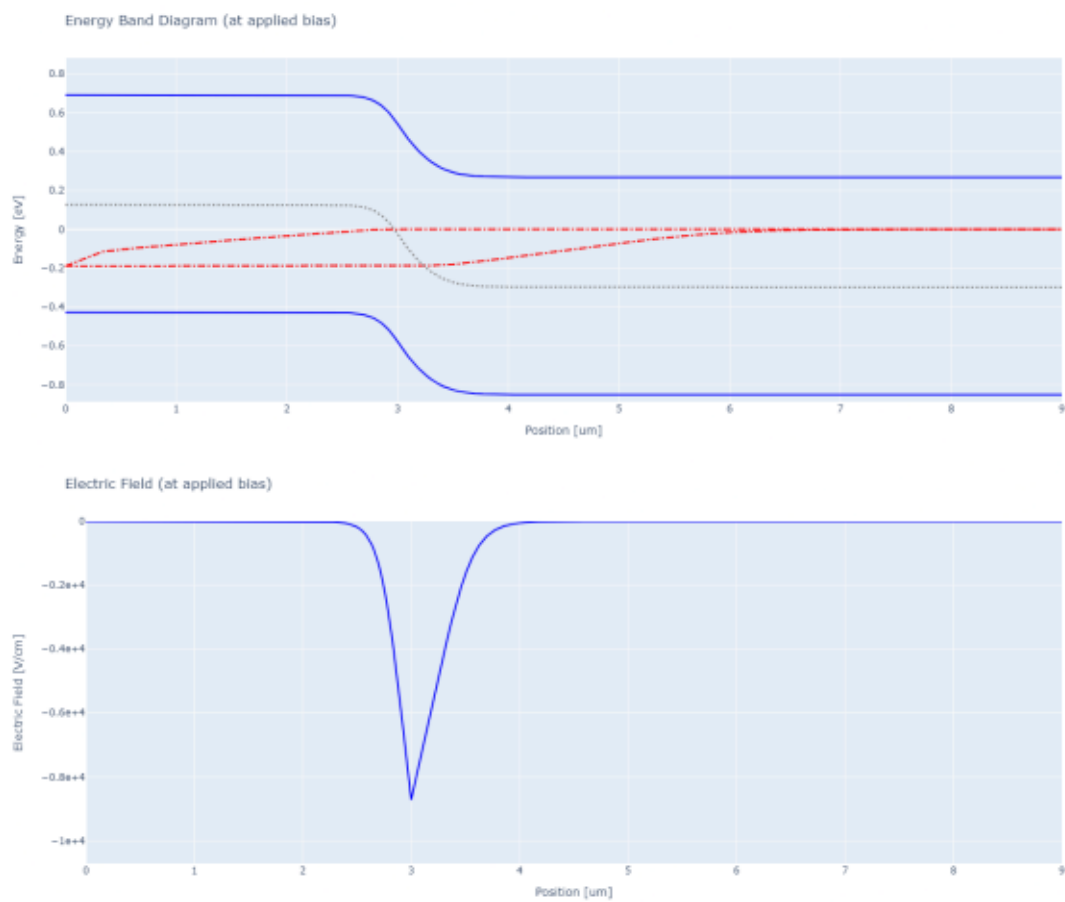


Figure 4: non equilibrium

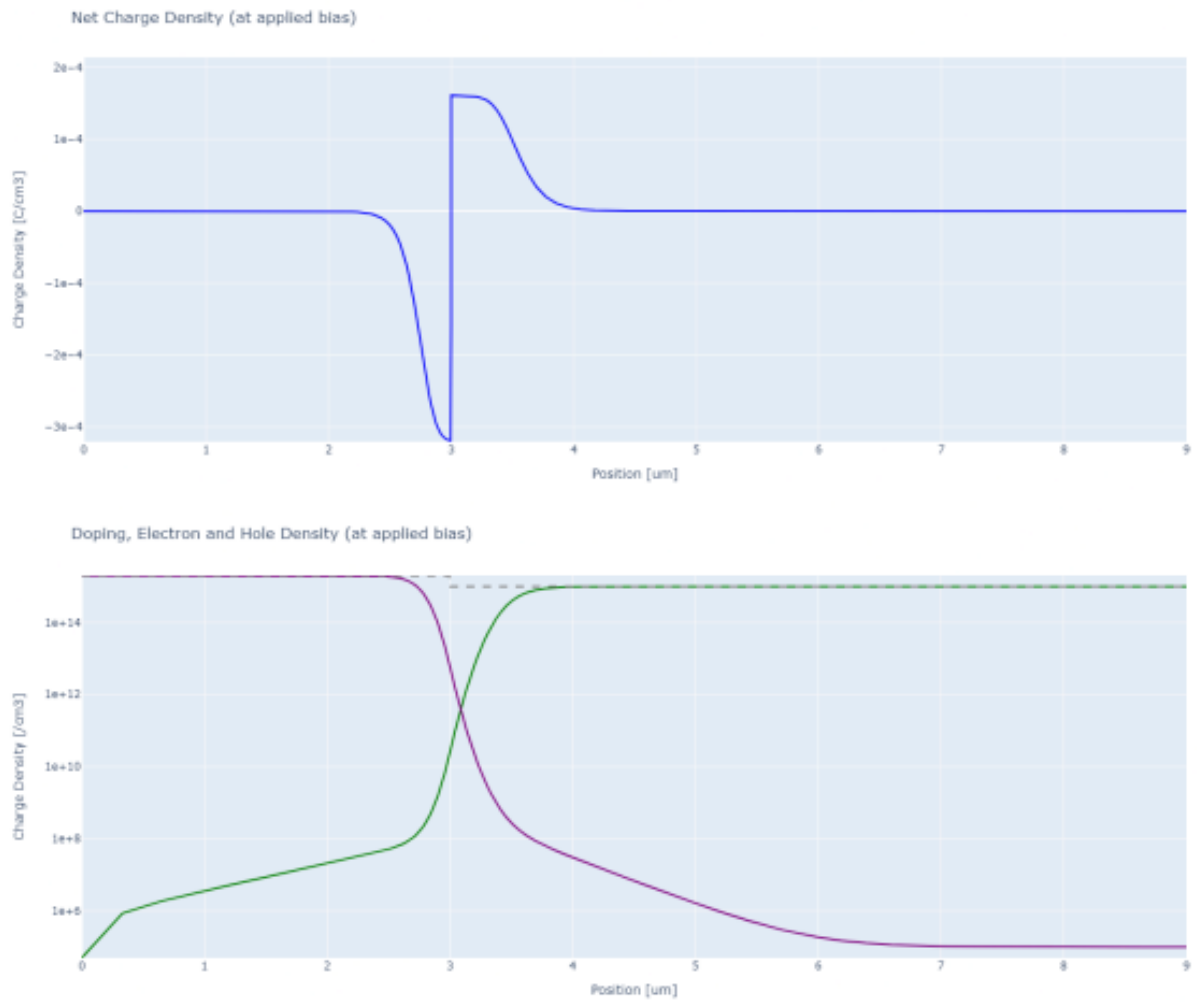


Figure 5: non equilibrium